

M.Sc. (Electronics) (NEP Pattern) Semester-I
NEP-31 / PSCELT101-Paper-I : Semiconductor Devices and Electronics Circuits

P. Pages : 2

Time : Three Hours



GUG/W/24/15087

Max. Marks : 80

-
- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and label diagrams wherever necessary.

Either:

1. a) Explain the action of bipolar junction transistor. 8
b) Explain the CB, CC and CE configurations of a transistor. 8

OR

- c) Explain terms thermal instability and bias stabilization of transistor. 8
d) Explain analysis of transistor as an amplifier using h-parameter. 8

Either:

2. a) Explain frequency response of RC-coupled amplifiers. 8
b) Explain application of BJT at high frequency. 8

OR

- c) Explain working of transformer coupled amplifier. 8
d) Write down difference between single stage and multistage amplifier. 8

Either:

3. a) Explain working of transformer coupled class-A power amplifier. 8
b) Explain class-B push pull amplifier. 8

OR

- c) Write down principle of feedback amplifiers, Explain difference between positive and negative feedback. 8
d) Explain effect of negative feedback in terms of gain stability. 8

Either:

- | | | | |
|-----------|----|--|----------|
| 4. | a) | Explain working of Phase Shift Oscillators. | 8 |
| | b) | Draw neat circuit diagram of Wien's Bridge oscillator and explain its working. | 8 |

OR

- | | | | |
|-----------|----|---|----------|
| | c) | Write down difference between Hartley and Colpitts oscillators. | 8 |
| | d) | Explain the working of crystal oscillators. | 8 |
| 5. | | Write short notes on each of the following: | |
| | a) | Write down application of transistor. | 4 |
| | b) | Write a short note on multistage amplifier. | 4 |
| | c) | Write a short note on classification of amplifier. | 4 |
| | d) | Explain working of crystal oscillators. | 4 |
