

M.Sc. F.Y. (Electronics) (NEP Pattern) Semester-I
NEP-32 / PSCELT102 - Paper-II : Analog and Digital System

P. Pages : 2

Time : Three Hours



GUG/W/24/15088

Max. Marks : 80

-
- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and label diagram wherever necessary.

Either:

1. a) Draw the circuit diagram of two stages RC coupled transistor amplifier. Explain its working. 8
- b) What is FET amplifier? Explain construction and working of FET amplifier. 8

OR

- c) What is multistage amplifier? Explain working and application multistage amplifier. 8
- d) What is current mirror circuit? Explain its specification and limitation. 8

Either:

2. a) Explain block diagram of Phase Lock Loop (PLL). 8
- b) Explain OPAMP as Wave-Shaping circuit. 8

OR

- c) State differences between oscillator and amplifier. Explain the construction and working of Schmitt trigger circuit. 8
- d) Explain application of OPAMP as an 8
- i) Integrator ii) Differentiator

Either:

3. a) Explain 4x4 keyboard encoder. 8
- b) Draw the state diagram of a DFF and obtained its characteristics equation. Draw the timing diagram. 8

OR

- c) What is decoder? Describe working of 4-bit binary decoder. 8
- d) Compare the Mealy and Moore Models using typical state diagram. 8

Either:

- | | | | |
|-----------|----|-----------------------------------------------------------|----------|
| 4. | a) | What is CPLD? Draw and explain the block diagram of CPLD. | 8 |
| | b) | What is FPGA? Draw its block diagram and explain. | 8 |

OR

- | | | | |
|-----------|----|--------------------------------------------------------------------------|----------|
| | c) | Discuss the architecture of Programmable Logic Array (PLA). | 8 |
| | d) | Discuss architecture of ROM in details. | 8 |
| 5. | | Solve the following. | |
| | a) | Explain frequency response of multistage amplifier and define bandwidth. | 4 |
| | b) | What is frequency to voltage converts? Explain. | 4 |
| | c) | Explain difference between decoder and demultiplexer. | 4 |
| | d) | Describe the methods of packaging of CPLDs. | 4 |
