

B.Sc. F.Y. (CBCS Pattern) Semester-I
USELT02 - Electronics-II - Semiconductor Diodes and Analog Electronics

P. Pages : 2

Time : Three Hours



GUG/W/24/11549

Max. Marks : 50

-
- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and well labelled diagram wherever necessary.
 3. Use of log table/calculator is allowed.

1. a) Explain the formation of depletion region in p-n junction diode. 6
- b) Differentiate between ideal and practical p-n junction diode. 4

OR

- c) Explain the formation of I-V characteristics of p-n junction diode. 5
- d) Explain avalanche breakdown mechanism in p-n junction diode. 5
2. a) Draw the circuit diagram of full wave rectifier using centre tap transformer and explain its working with its input and output waveform. 6
- b) What is filter? Explain the role of filter in power supply. 4

OR

- c) Explain the working of half wave rectifier with suitable diagram. State its disadvantages. 5
- d) Explain Zener diode as voltage regulator with suitable circuit diagram. 5
3. a) Explain the forward characteristics of CE configuration with suitable diagram. 5
- b) Define α and β Derive the relation between α and β . 5

OR

- c) Explain the fixed biasing method of BJT. State its disadvantages. 5
- d) What is thermal runaway? How can it be avoided? 5

Either:

4. a) Explain transistor as a two port network. 5
- b) Draw the hybrid equivalent circuit of common emitter configuration and explain it. 5

OR

- c) Derive the expression for input impedance and current gain of CE configuration in terms of h-parameters. 5
- d) Draw the hybrid equivalent circuit of CB configuration with proper notation and explain it. 5

5. Solve **any ten** question of the followings: **1x10**

- a) What is p-n junction diode?
- b) Define reverse saturation current of p-n junction diode.
- c) State the application of p-n junction diode.
- d) Draw the circuit diagram of bridge rectifier.
- e) Define load regulation.
- f) Define ripple factor.
- g) Draw the circuit diagram of CB configuration.
- h) What is DC load line?
- i) Define stability factor S.
- j) What is two port network?
- k) What is h_{11} and h_{12} ?
- l) State the advantages of h-parameter?
