

B.Sc. (New CBCS Pattern) Semester - II
USELT03 - Electronics Paper-I
(Unipolar Devices and Linear Integrated Circuits)

P. Pages : 2

Time : Three Hours



GUG/S/23/11578

Max. Marks : 50

-
- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw well labelled diagrams wherever necessary.
 3. Use of calculator and log table is allowed.

Either:

1. a) Explain Construction and working of N-channel JFET. 5
- b) Draw I-V Characteristics of JFET and explain. 5

OR

- c) Explain construction and working of MOSFET. 5
- d) State the advantages and disadvantages of MOSFET. 5

Either:

2. a) Explain the construction of transformer coupled amplifier with suitable diagram. 5
- b) Explain Concept of feedback. What is positive and negative feedback? State advantages of negative feedback. 5

OR

- c) Explain construction of two stage RC coupled amplifier. 5
- d) Differentiate between Class A, and B amplifiers. 5

Either:

3. a) Explain construction and working of difference amplifier. 5
- b) Explain the needs of two power supplies in difference amplifier. 5

OR

- c) Draw the block diagram of Op-amp (IC 741) and explain the function of each block in it. 6
- d) Define 4
 - i) CMRR
 - ii) Slew rate.

Either:

4. a) Explain Op-amp as an inverting amplifier. 5
- b) In Op-amp as an inverting amplifier if $R_i = 10 \text{ Kohm}$ and $R_f = 100 \text{ Kohm}$ then find the feedback gain of amplifier. 5

OR

- c) Explain Op-amp as in Integrator. 5
- d) Explain Op-amp as a differentiator. 5
5. Attempt **any ten** of the followings. 10
- a) What is Pinch off voltage?
- b) Draw symbol of MOSFET.
- c) Define drain resistance.
- d) Define frequency response in amplifier.
- e) State advantage of positive feedback.
- f) State advantage of Class C amplifier.
- g) Define input offset current in Op-amp.
- h) Define open loop gain in Op-amp.
- i) Define common mode gain.
- j) What is virtual ground?
- k) Write the formula for gain with feedback in non-inverting amplifier.
- l) If input voltage in unity gain amplifier is 10 V then what will be the Output voltage?
