

B.Sc. F.Y. (CBCS Pattern) Semester - I
USELT02 - Electronics Paper -II
(Semiconductor Diodes and Analog Electronics)

P. Pages : 2

Time : Three Hours



GUG/S/23/11549

Max. Marks : 50

Either:

1. a) What is PN junction? Explain the formation of PN junction? Define Internal potential Barrier. **10**

OR

- b) With the help of circuit diagram explain the forward bias characteristics of PN junction diode? Explain the importance of VI characteristics. **10**

Either:

2. a) What is rectifier? With the help of circuit diagram explain the working of half wave rectifier? Draw also input and output wave forms? **10**

OR

- b) What is filter? Explain with wave forms working of shunt capacitor filter. Define load and line regulation. **10**

Either:

3. a) With suitable diagram explain the input output of transistor in CE mode configuration. What is the importance of output characteristic? **10**

OR

- b) What is biasing? With the help of diagram explain potential difference method of biasing. What is thermal runaway? **10**

Either:

4. a) What is two port networks? Explain how we find $h_{11}, h_{12}, h_{21}, h_{22}$, Define voltage gain and frequency response? **10**

OR

- b) Draw the small signal ac equivalent circuit diagram of RC coupled amplifier and derive h parameter for voltage gain, input impedance, current gain. **10**

5. Attempt **any ten** of the followings.

10

- a) Define pinch off voltage.
- b) What is Schottky diode?
- c) Define dynamic forward resistance of the diode.
- d) What is ripple factor?
- e) What is the efficiency of full wave rectifier?
- f) Differentiate half wave and full wave rectifier.
- g) Define Current amplification factor.
- h) Define stability Factor.
- i) What is Q point?
- j) What is h parameter?
- k) Define input impedance.
- l) Why h parameter is called Hybrid parameter?
