

B.E. Electrical (Electronics & Power) Engineering (Model Curriculum) Semester - IV
SE202 - Digital Electronics

P. Pages : 2

Time : Three Hours



GUG/S/23/13804

Max. Marks : 80

-
- Notes : 1. All questions carry marks as indicated.
2. Assume suitable data wherever necessary.
3. Illustrate your answers wherever necessary with the help of neat sketches.

1. a) State De-Morgan's theorems. 4
- b) Convert the following binary numbers into decimal, octal and hexadecimal: 6
- i) $(11010101)_2$
- ii) $(11010011)_2$
- c) Prove NOR gate is universal gate. 6

OR

2. a) Subtract 14-25 using 1's compliment. 4
- b) Find the complement of the function. 4
- i) $F1 = XYZ' + X'YZ$
- ii) $F2 = X(YZ' + Y'Z)$
- c) Explain CMOS NAND gate 8
3. a) Minimize using K-Map $F = \Pi M (0, 6, 9, 10, 13)$. d (1, 3, 8) 4
- b) Realize Full Adder using two half Adder. 6
- c) Design 1-bit comparator. 6

OR

4. a) Design 3-bit Binary to Grey Code Converter. 8
- b) Minimize the function using QuineMcClusky $F=S (1, 2, 5, 6, 7, 9, 10, 11, 14)$ 8
5. a) What is race around condition in JK flip flop? How it can be avoided. 4
- b) Convert D flip flop to T Flip Flop. 6
- c) Explain 3-bit ring counter. 6

OR

6. a) Explain SR Flip Flop give its Characteristics Table, Characteristic Equation and Excitation table. **8**
- b) Design a type T synchronous counter that goes through states 0, 3, 5, 6, 0 ----. Is the counter self starting? If the counter is not self starting suggest a suitable modification to remove the lock-out **8**
7. a) Explain 3 bit R-2R ladder DAC. **8**
- b) Explain different specification of DAC. **8**

OR

8. a) Explain flash type ADC with its advantage and disadvantages. **8**
- b) Describe Dual slope type ADC. **8**
9. a) Explain the classification and characteristic of memory. **8**
- b) Explain how read and write operation is performed in memory with suitable diagram. **8**

OR

10. a) Design a 3-bit binary to excess-3 convertor using PROM. **8**
- b) What is PLA? Implement the following function using PLA **8**
- i) $F1 = \sum m(0, 3, 4, 7)$
- ii) $F2 = \sum m(1, 2, 5, 7)$
