

M.Sc.(Physics) (CBCS Pattern) Semester - III
PSCPHYT11-4 - Paper-II (Core Elective E1.4) : Applied Electronics-I

P. Pages : 2

Time : Three Hours



GUG/S/23/11301

Max. Marks : 80

Either:

1. a) What is multivibrator? Compare monostable and astable multivibrators with suitable circuit diagrams. 8
- b) Explain inverting and non-inverting amplifiers. 8

OR

- e) Draw the block diagram of a typical operational amplifier and explain the function of each block. Also explain open loop configuration of Op-Amp. 8
- f) Define Barkhausen criteria for oscillations. Draw circuit diagram for Weinbridge oscillator, explain its working. 8

Either:

2. a) What is modulation? Explain amplitude modulation. 8
- b) Discuss the use of antennas in microwave communication system. 4
- c) Explain in brief Fresnel zone problem with respect to microwave communication. 4

OR

- e) Explain the atmospheric effect on the propagation of microwave. 6
- f) Discuss ground reflection with respect to microwave communication. 4
- g) What is Demodulation? Explain demodulation of AM waves. 8

Either:

3. a) Explain the working of R-2R ladder D/A converter with suitable diagram. 8
- b) Discuss read only memory (ROM) and random access memory (RAM). 6
- c) What is de-multiplexing. 2

OR

- e) What is microprocessor? Explain about stack and subroutines. 8
- f) Draw Pin diagram of IC 8085, microprocessor and label all pins clearly. 8

Either:

- | | | | |
|-----------|----|---|----------|
| 4. | a) | What is gunn effect? Discuss principle operation of gunn diode. | 8 |
| | b) | Discuss the working of Helix travelling wave tubes. | 8 |

OR

- | | | | |
|-----------|----|--|----------|
| | e) | What are microwave devices? Explain Klystrons used as microwave devices. | 8 |
| | f) | Write a note on IMPATT and TRAPATT diode. | 8 |
| 5. | | Attempt all the following. | |
| | a) | Explain LC tunable oscillator. | 4 |
| | b) | Write a note on detector components in microwave communication. | 4 |
| | c) | Discuss assembly language programmes. | 4 |
| | d) | Explain velocity modulation. | 4 |
