

B.Sc.-II (CBCS Pattern) Semester - III  
**USELT05 - Electronics Paper-I : Power Amplifier, Oscillators and Power Supplies**

P. Pages : 2

Time : Three Hours



**GUG/S/23/11604**

Max. Marks : 50

- 
- Notes :
1. All questions are compulsory and carry equal marks.
  2. Use of log table/calculator is allowed.
  3. Draw neat and well labelled diagram wherever necessary.

**Either:**

1. a) Differentiate between power amplifier and voltage amplifier. **4+6**

Explain the transformer coupled class A power amplifier with suitable circuit diagram.  
Derive the expression for its efficiency.

**OR**

- b) Draw the circuit diagram of class B push pull amplifier and explain its working. **6+4**

Explain the working of complementary symmetry amplifier.

**Either:**

2. a) Explain the working of phase shift oscillator with suitable diagram. **4+6**

Explain the construction and working of Wein bridge oscillator.

**OR**

- b) Draw the circuit diagram of Colpitt's oscillator and explain its working. **5+5**

Explain the working of L-C oscillator circuit with suitable circuit diagram.

**Either:**

3. a) Draw the block diagram of unregulated DC power supply and explain each block. **5+5**

Explain Zener diode as a voltage regulator with suitable circuit diagram.

**OR**

- b) Explain the working of series pass regulator with suitable circuit diagram. **6+4**

Differentiate between series and shunt type regulator.

**Either:**

4. a) Draw the functional block diagram of IC LM317 and explain the function of each block. **7+3**  
State the advantages of three terminal voltage regulator.

**OR**

- b) Draw the circuit diagram of regulated +5V power supply using IC78XX and explain its working. **5+5**

Draw the circuit diagram of dual power supply of 12V using IC78XX and IC79XX and explain it.

5. Solve **any ten** of the followings: **1x10**

- a) What is power transistor?
- b) What is efficiency of amplifier
- c) State disadvantages of class A amplifier with resistive load?
- d) What is oscillator?
- e) State Barkhausen Criteria for oscillation.
- f) State applications of oscillator.
- g) State the disadvantages of DC unregulated power supply?
- h) What is DC regulated power supply?
- i) Define line regulation.
- j) State the specification of IC LM 317
- k) What is dual power supply?
- l) Draw the pin configuration of IC 79XX?

\*\*\*\*\*