

M.Sc. (Physics) (NEP Pattern) Semester-I
NEP-233 / 01MSCPH1 - DSC Paper-I - Semiconductor Physics and Devices

P. Pages : 2

Time : Three Hours



GUG/S/25/15134

Max. Marks : 80

Either:

1. a) Explain construction, working Characteristics of Unijunction Transistor (UJT). 8
- b) Explain the working of N-channel JFET. Discuss the output characteristics of N-channel JFET in details. 8

OR

- e) Explain the working of LED and photo-diode. 8
- f) Explain construction and working of SCR.. 8

Either:

2. a) What is Oscillator? Explain the Colpitts Oscillators with diagram in detailed. 8
- b) Explain Transformer-Coupled amplifier and its frequency response graph. What are the advantages of it? 8

OR

- e) Explain the construction of Hartley Oscillator and find the expression for frequency of Oscillator. 8
- f) Explain construction of Bipolar Junction Transistor (BJT). Discuss the input and output characteristics of CB connection. 8

Either:

3. a) Explain working of Op-Amp as integrator and differentiator. 8
- b) What is subtractor? Give truth table and draw the circuit diagrams of half and full subtractor. 8

OR

- e) What are the types of multivibrators? Explain the construction and working of bistable multivibrator. 8
- f) How the inverting and non-inverting configurations are useful as summing, scaling and averaging amplifiers. 8

Either:

4. a) What are magnetrons? Explain the principle of operation of magnetrons? 8
- b) Explain the construction and working of IMPATT and TRAPATT diode. 8

OR

- e) Discuss the Klystrons. Explain basic principles of two cavity klystrons and reflex klystrons. 8
- f) Explain working of Helix travelling wave tube. 8
5. Attempt all the following questions.
- a) Explain the working of n-channel enhancement MOSFET. 4
- b) Discuss the three basic logic gates. 4
- c) Explain the use of Op-Amp as subtractor. 4
- d) Explain velocity modulation. 4
