

M.Sc. (Electronics) (NEP Pattern) Semester-I  
**NEP-31 / PSCELT101-Paper-I : Semiconductor Devices and Electronics Circuits**

P. Pages : 2

Time : Three Hours



**GUG/S/25/15087**

Max. Marks : 80

- 
- Notes : 1. All questions are compulsory and carry equal marks.  
2. Draw neat and labelled diagram wherever necessary.

**Either:**

1. a) Explain the construction and working of BJT. 8  
b) Draw I/P and O/P V-I characteristics of BJT and Explain. 8

**OR**

- c) Explain the analysis of transistor amplifier in CE configuration using h-parameters. 8  
d) Explain the need of bias stabilization. 8

**Either:**

2. a) Explain working of RC coupled amplifier and draw the frequency response curve. 8  
b) Draw the circuit diagram of transformer coupled amplifier and explain its working. 8

**OR**

- c) Describe high frequency performance of Bipolar junction transistor. 8  
d) Differentiate between RC couple and transformer couple amplifier. 8

**Either:**

3. a) Draw the circuit diagram of transformer couple class A power amplifier and explain its working. 8  
b) Derive the expression for the efficiency of transformer coupled Class A power amplifier. 8

**OR**

- c) Explain the working of class B push pull amplifier with neat circuit diagram. What is cross-over distortion: How does it can be removed. 8  
d) What is power amplifier? State difference between single tuned amplifier and double tuned amplifier. 8

**Either:**

- |           |    |   |          |
|-----------|----|---|----------|
| <b>4.</b> | a) | Explain the construction and working of phase shift oscillator. State its advantages.                   | <b>8</b> |
|           | b) | Explain the construction and working of Wein bridge oscillator. State its advantages and disadvantages. | <b>8</b> |

**OR**

- |           |    |   |          |
|-----------|----|---|----------|
|           | c) | Draw the circuit diagram of transistor Colpitts oscillator circuit and explain its working. | <b>8</b> |
|           | d) | Explain the working of crystal oscillator and state its advantages and disadvantages.       | <b>8</b> |
| <b>5.</b> |    | Solve the followings.   |          |
|           | a) | Describe cascaded transistors?  | <b>4</b> |
|           | b) | State and explain the drawbacks of RC coupled amplifier.                                    | <b>4</b> |
|           | c) | Explain the effect negative feedback.   | <b>4</b> |
|           | d) | Explain the construction of Hartley Oscillator.   | <b>4</b> |

\*\*\*\*\*