

M.Sc. (Electronics) (NEP Pattern) Semester-I
NEP-32 / PSCELT102 - Paper-II : Analog and Digital System

P. Pages : 2

Time : Three Hours



GUG/S/25/15088

Max. Marks : 80

-
- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and label diagrams wherever necessary.

Either :

1. a) Design a differential amplifier using field effect transistor. 8
b) What is a current Mirror? How it is used in impedance matching? 8

OR

- c) Explain analysis of BJT for multistage amplifiers? 8
d) Explain the Common Source amplifier with active Loads? 8

Either :

2. a) Explain Operational Amplifiers (OPAMP) as a differentiator and derive the expressions for its output voltage. 8
b) Explain Schmitt trigger circuit. 8

OR

- c) Explain the voltage-to-current converter circuit using Op-amp. What are its applications? 8
d) What is Phase locked loop (PLL)? Draw and explain its use as a frequency synthesizer. 8

Either :

3. a) Explain 4x4 keyboard encoder. 8
b) Explain Sequential circuits? Draw state diagrams, characteristic equation of D-flip-flops. 8

OR

- c) Explain the difference between synchronous and asynchronous counters. Design a 3 bit ripple counter using TFFS. 8
d) Describe of counters with lockout prevention. 8

Either :

4. a) Explain the design of a sequence detector circuit. 8
b) Explain the steps involved in design of ALU in digital circuits using logic gates. 8

OR

- c) What is a PLA? Show how PLA can be programmed to implement the sum and carry outputs of a full adder? 8
- d) What is CPLD? How is it different from FPGA? State advantage of using CPLDs. 8
- 5. Solve the followings:
 - a) Explain small signal circuit analysis. 4
 - b) What is active filter? Explain. 4
 - c) State difference between combinational and sequential circuits. 4
 - d) Write a note on ring counter. 4
