

M.Sc. - II (Electronics) (NEP Pattern) Semester-IV
PSCELT402 - Paper-II : Network Analysis and Synthesis

P. Pages : 2

Time : Three Hours




GUG/S/25/16340

Max. Marks : 80

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw a neat and Labeled diagram and use supporting data wherever necessary.
 3. Avoid vague answers and write specific points/answers related questions.

Either:

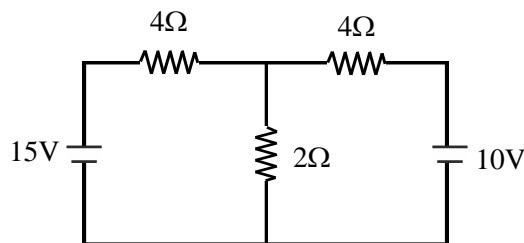1. a) What is mesh analysis? Find current through $2\ \Omega$ resistor in the following figure using mesh analysis. **8**



- b) Explain the nodal analysis method for solving a network. **8**

OR

- c) Explain the following **8**

- | | |
|-------------------|-------------------------------|
| i) Planner graph, | ii) Tree |
| iii) Cotree | iv) Reduced incidence matrix. |

- d) What is source transformation? Explain the conversion method of voltage source to current source and vice versa with example. **8**

Either:

2. a) State and prove superposition **8**

- b) State and prove reciprocity theorem. **8**

OR


- c) Explain the star – delta and delta – star transformation in the network. **8**

- d) State and prove Millman's theorem. **8**

Either:

3. a) Discuss the Heaviside's expansion theorem with suitable example. **8**

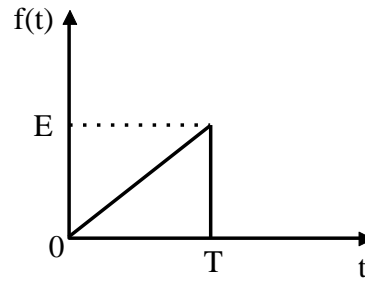- b) Determine the Laplace transform of saw – tooth waveform shown in following Figure. 8



OR

- c) Find the inverse transform of the function 8

$$F(s) = \frac{1}{(s+1)^4} + \frac{s-3}{(s-3)^2 + 6}$$

- d) State and explain initial value theorem.

Either:

4. a) Explain time domain behavior from Pole zero plot. 8

- b) Describe Hurwitz polynomials with suitable examples. 8

OR

- c) Describe the synthesis of RC network by Foster method. 8

- d) Describe the Routh-Hurwitz criterion. 8

5. Attempt the followings:

- a) Explain State variable analysis. 4

- b) What is duality of network? Explain. 4

- c) Explain partial function expansion. 4

- d) A linear System is described by the differential equation. 4

$$\frac{d^2y}{dt^2} + 5\frac{dy}{dt} + by = \frac{2dy}{dt} + 1$$

Find the system poles and zeros.
