

M.Sc. - I (Electronics) (NEP Pattern) Semester-I  
**NEP-31 / PSCELT101-Paper-I : Semiconductor Devices and Electronic Circuits**

P. Pages : 1

Time : Three Hours



**GUG/W/23/15087**

Max. Marks : 80

- 
- Notes : 1. All questions are compulsory and carry equal marks.  
2. Draw neat and well-labelled diagrams wherever necessary.

- |    |     |  |   |
|----|-----|--|---|
| 1. | a)  | Determine the following parameter of the stage CE configuration using the h-parameter                    | 8 |
|    | i)  | Current Gain   |   |
|    | ii) | Voltage Gain   |   |
|    | b)  | Explain the input and output characteristics of CB configuration.  | 8 |
|    |     | <b>OR</b>  |   |
|    | c)  | Explain the CE hybrid model with a suitable diagram.   | 8 |
|    | d)  | Explain the need of bias stabilization.  | 8 |
| 2. | a)  | Explain the working of the CE amplifier with respect to high frequency.                                  | 8 |
|    | b)  | Explain the mid-range frequency response of RC couple amplifier.   | 8 |
|    |     | <b>OR</b>  |   |
|    | c)  | Derive an expression for the voltage amplification of RC couple transistor amplifier for high frequency. | 8 |
|    | d)  | Differentiate between RC couple and transformer couple amplifier.  | 8 |
| 3. | a)  | Explain the construction and working of Transformer coupled class A amplifier.                           | 8 |
|    | b)  | Derive the expression for the efficiency of transformer coupled class A amplifier.                       | 8 |
|    |     | <b>OR</b>  |   |
|    | c)  | Explain the construction and working of class B push pull amplifier.                                     | 8 |
|    | d)  | Discuss the double tune amplifier.   | 8 |
| 4. | a)  | Discuss the feedback requirement for oscillations.   | 8 |
|    | b)  | Explain the construction and working of phase shift oscillator.  | 8 |
|    |     | <b>OR</b>  |   |
|    | c)  | Explain the working of Wein bridge oscillator with suitable circuit diagram.                             | 8 |
|    | d)  | Draw and explain crystal oscillator. State its advantages.   | 8 |
| 5. | a)  | Discuss the transistor action.   | 4 |
|    | b)  | Explain the thermal instability.   | 4 |
|    | c)  | State the advantages of negative feedback.   | 4 |
|    | d)  | Explain the working of Colpitt's oscillator.   | 4 |

\*\*\*\*\*