



5. a) Explain 3 $\phi$  bridge inverter operation for 180° mode of operation with relevant phase voltage waveform. **8**
- b) Draw a modified series inverter circuit. Explain qualitatively how you can have output frequency higher than series resonance frequency. **8**

**OR**

6. a) Compare 180° and 120° conduction mode of 3 phase bridge inverter. **8**
- b) Explain the operation of single-phase bridge inverter with the help of load, voltage and load current waveforms. **8**
7. a) Draw the schematics of step-down chopper. Explain its working and derive an expression for output voltage in terms of duty-cycle for a step-down chopper. **8**
- b) A chopper circuit is operating on TRC principle at a frequency of 1 kHz on a 220 V d.c. supply. If the load voltage is 180V, calculate the conducting and blocking period of thyristor in each cycle. **8**

**OR**

8. a) With the help of a circuit diagram, explain the working of class D chopper. **8**
- b) A step down dc chopper has a resistive load of  $R = 15 \text{ ohm}$  and input voltage  $E_{dc} = 200\text{V}$ . When the chopper remains ON, its voltage drop is 2.5 V. The chopper frequency is 1 kHz. If the duty cycle is 50%, determine :
- |                           |  |
|---------------------------|--|
| i) Average output voltage | ii) RMS output voltage                     |
| iii) Chopper efficiency   | iv) Effective input resistance of chopper. |
9. a) Draw and explain the necessity of static and dynamic equalizing circuit for series connected SCRs? Derive relations used for determining the values of shunt resistor R and capacitor C in this circuit. **8**
- b) What are the problems associated with firing of parallel connected SCRs? Draw and explain circuit for firing of parallel connected SCRs. **8**

**OR**

10. a) What do you mean by Snubber circuit? Draw and explain the function of each component. **8**
- b) What are the different methods of triggering SCRs in series? Draw and explain sequential firing circuit for triggering of series connected SCRs. **8**

\*\*\*\*\*