

B.Sc. New CBCS Pattern Semester-II
USELT04 - Electronics Paper-II (Digital Integrated Circuit)

P. Pages : 2

Time : Three Hours



GUG/W/23/11579

Max. Marks : 50

-
- Notes : 1. All questions are compulsory and carry equal marks.
2. Draw neat and labelled diagram wherever necessary.

Either:

1. a) State the difference between Half adder and full adder? Write down the truth table for half adder and explain how it will implement using gates? **5+5**

OR

- b) What is encoder? Explain the working of decimal to BCD encoder using logic gates. Draw the logic diagram of 2:1 mux using basic gates. **5+5**

Either:

2. a) Draw the block diagram of IC 555 timer and explain the function of each block. Draw the circuit diagram of astable multivibrator using IC – 555. **7+3**

OR

- b) Draw the logic diagram of D-Flip flop and explain its working with truth table. What is race around condition in JK Flip Flop? **7+3**

Either:

3. a) What is counter? Explain the working of 4-bit binary counter with truth table. Also draw the timing diagram. **10**

OR

- b) What is ring counter? Explain the working of Johnson counter with the help of timing diagram and truth table. **3+7**

Either:

4. a) What is register? Describe the construction and working of SISO shift register. Draw the timing diagram. **10**

OR

- b) What is D/A converter? Explain the working of R-2R ladder D/A converter. **10**

5. Attempt **any ten** of the following:

1x10
=10

- a) What is SOP and POS?
- b) Define Decoder?
- c) What is K-Map?
- d) State the use of preset and clear input.
- e) Draw the logic diagram of RS Flip Flop using NAND gate.
- f) What is an edge triggered Flip Flop?
- g) State the application of counter.
- h) What is modulus of counter?
- i) What is Asynchronous counter?
- j) Draw circuit of Sample and hold circuit.
- k) State two drawbacks of single slope converter.
- l) Define accuracy of A/D converter.
