

B.Sc. - I New CBCS Pattern Semester-II
USELT03 - Electronics Paper-I
(Unipolar Devices and Linear Integrated Circuits)

P. Pages : 2

Time : Three Hours



GUG/W/23/11578

Max. Marks : 50

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and labeled diagram wherever necessary.
 3. Use of calculator/ log table is allowed.

Either:

1. a) Explain the construction and working of N channel junction field effect transistor. **7+3**
Differentiate between FET and BJT.

OR

- b) Explain the construction and working of DE MOSFET. **6+4**
Explain JFET as a amplifier.

Either:

2. a) Explain the Class A, Class B and Class C amplifier with respect to conduction of current with suitable diagram. **6+4**
Draw the circuit diagram of direct coupled amplifier and explain its working.

OR

- b) Explain the construction and working of transformer coupled amplifier. **5+5**
What is feedback? Explain positive and negative feedback.

Either:

3. a) Draw the circuit diagram of difference amplifier and explain its working. **7+3**
State the advantages of difference amplifier.

OR

- b) Differentiate between direct couple (DC) amplifier and operational amplifier. **4+6**
Explain the need of dual power supply to difference amplifier.

Either:

4. a) Explain the op-amp as an inverting amplifier with suitable diagram. **6+4**
Explain the concept of virtual ground in op-amp.

OR

- b) Draw the circuit diagram of op-amp as an adder and explain. Derive the expression for its output voltage. **4+6**
Explain the working of zero crossing detector with suitable diagram.

5. Attempt **any ten** of the followings.

10x1

- a) State the advantages of FET.
- b) Differentiate between FET and MOSFET.
- c) Draw the symbol of UJT.
- d) State the advantages of transformer coupled amplifier.
- e) State advantages of negative feedback?
- f) Draw the frequency response of RC coupled amplifier.
- g) What is operational amplifier?
- h) Give any four ideal characteristics of op-amp.
- i) Define CMRR.
- j) What is unity gain amplifier?
- k) Draw the circuit diagram of integrator using op-amp.
- l) State the applications of op- amp?
