

M.Sc.(Electronics) (NEP Pattern) Semester-I
NEP-32 / PSCELT102 - Paper-II - Analog and Digital System

P. Pages : 2

Time : Three Hours



GUG/W/23/15088

Max. Marks : 80

- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw a neat and labeled diagram and use supporting data wherever necessary.
 3. Avoid vague answers and write specific points/answers related questions.

Either:

1. a) What is BJT differential amplifier? Explain construction & working of dual input differential amplifier. 8
- b) What is Multistage Amplifier? Explain working and applications of multistage amplifier. 8

OR

- c) Draw the circuit diagram of two stages RC coupled transistor amplifier. Explain its working. 8
- d) Obtain an expression for Current Gain, Voltage and Power Gain. 8
In an amplifier, when the signal changes by 0.04 V, the base current changes by $15\mu\text{A}$ and collector current changes by 2 mA. If $R_L = 10\text{K}$ and $R_C = 8\text{K}$, find: (i) Current gain, (ii) Input impedance, (iii) Voltage gain and (iv) Power gain.

Either:

2. a) Explain the use of OPAMP as an (i) Integrator and (ii) Differentiator. 8
- b) Explain the use of OPAMP as (i) a Switching Circuit and (ii) Schmitt trigger circuit. 8

OR

- c) Explain the block diagram of Phase Locked Loop (PLL). 8
- d) State the important characteristics of OPAMP. How you will use OPAMP as an inverting amplifier? State its limitations in inverting mode. 8

Either:

3. a) What is encoders and decoders? Describe working of 4-bit binary decoder. 8
- b) Map the following expression and simplify them using K-map. 8
 - i) $ABC + \bar{A}B\bar{C} + B$
 - ii) $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + ABCD + A\bar{B}C\bar{D}$

OR

c) Explain working of multiplexer and De-multiplexer. 8

d) Explain working of 4-bit ripple counter. 8

Either:

4. a) What is digital system design? Explain the concept to design system for control unit. 8

b) Explain the concept to design system for sequence detector and sequence generator. 8

OR

c) Explain the working of ring counter with waveforms. 8

d) Describe PLA with suitable diagram. 8

5. Solve all questions.

a) Explain frequency response of multistage amplifiers and define the band width. 4

b) What is a Voltage to Current Converter? 4

c) What is Mod Counter? Describe working of Asynchronous Mod-7 counter. 4

d) What is an arithmetic – logic unit (ALU)? Explain its role in digital system. 4
