

B.Tech. / B.E. Electrical (Electronics & Power) Engineering (Model Curriculum) Semester-III
103 / 003 - Analog Electronics Circuits

P. Pages : 2

Time : Three Hours



GUG/W/23/13854

Max. Marks : 80

- Notes :
1. All questions carry marks as indicated.
 2. Assume suitable data wherever necessary.
 3. Illustrate your answers wherever necessary with the help of neat sketches.

1. a) Draw and explain the V-I characteristics of Zener diode. **8**
b) Compare Halfwave, fullwave and Bridge wave rectifier. **8**

OR

2. a) Define : **8**
i) Efficiency. ii) Ripple factor.
iii) PIV. iv) TUF.
b) Draw and explain the operation of single stage common emitter transistor amplifier. **8**
3. a) What MOSFET. Draw and explain drain and transfer characteristics of n-channel depletion type MOSFET. **8**
b) Define: **8**
i) Drain Resistance (r_d).
ii) Transconductance (g_m)
iii) Amplification factor (μ).

OR

4. a) Draw and explain fixed bias circuit for MOSFET. **8**
b) Draw and explain common source MOSFET amplifier. **8**
5. a) Draw and explain the operation of Class 'B' push-pull power amplifier. **8**
b) Define: **8**
i) CMRR ii) Slew rate
iii) PSRR iv) Input bias current.

OR

6. a) What is operational amplifier. Explain the ideal characteristics of operational amplifier. **8**
b) What is multistage amplifier. Draw and explain the operation two stage direct coupled amplifier. **8**

7. a) Explain the working of op-amp inverting amplifier. Derive the expression for its voltage gain. **8**
- b) Explain the working of op-amp active differentiator. **8**

OR

8. a) Draw and explain op-amp PID controller. **8**
- b) What is oscillator. Explain the operation of op-amp wein bridge oscillator. **8**
9. a) What is multivibrator. Explain the operation of op-amp monoshot multivibrator. **8**
- b) Draw and explain half wave precision rectifier circuit. **8**

OR

10. a) Draw and explain triangular wave generator using op-amp. **8**
- b) With help of neat diagram and waveform explain the full wave precision rectifier. **8**
