



- Either:**
3. a) i) Explain the construction & working of NPN transistor. 4
- ii) With the neat circuit diagram, explain the characteristics of NPN transistor in common emitter mode. 4
- iii) Calculate the emitter current in transistor for which  $\beta = 50$  and  $I_B = 20\mu A$ . 2
- OR**
- b) i) Explain the working of transistor as a CE amplifier with graphical analysis. 2½
- ii) Compare class-A and class-B amplifier. 2½
- iii) Explain the working of RC coupled amplifier. 2½
- iv) For the transistor  $\alpha = 0.98$  which carries emitter current of 12mA. Find  $I_C, I_B$ . 2½
- Either:**
4. a) i) With the neat circuit diagram explain the working of difference amplifier. 6
- ii) Why difference amplifier needs two power supplies. 2
- iii) Define input bias current and input offset current. 2
- OR**
- b) i) Explain the working of OPAMP as an Integrator. 2½
- ii) Explain the working of OPAMP as an Adder. 2½
- iii) Explain the working of OPAMP as an inverting amplifier. 2½
- iv) Resistance of 1M ohm and capacitance of  $1\mu F$  is used for the OPAMP differentiator. 2½  
What would be noise voltage at the output of it if input noise frequency is 1 MHz and the amplitude of the input noise voltage is  $1\mu V$ .
5. Attempt **any ten** of the following.
- a) Draw the symbol for EX-OR gate and write its truth table. 1
- b) Draw the circuit diagram of Half subtractor. 1
- c) Draw the logical circuit for Boolean equation  $Y = AB + \bar{C}$ . 1
- d) What is Photocell? 1
- e) Define static resistance and dynamic resistance. 1
- f) Define rectifier. 1
- g) Define current gain  $\alpha$  and  $\beta$ . 1
- h) Define stability factor of transistor. 1
- i) A change of 200m V in base-emitter voltage causes change of  $100\mu A$  in the base current. Find input resistance of transistor. 1
- j) Define CMRR 1
- k) State characteristics of an ideal OPAMP. 1
- l) Give the pin configuration of OPAMP IC-741. 1

\*\*\*\*\*