

7. a) Compare CPLD and FPGA? **4**
- b) Draw and explain the architecture of a FPGA. **6**
- c) Draw CMOS inverter? Explain its operation in brief. **6**

OR

8. a) Define the following terms Fan in, Fan out, Propagation delay, Noise margin, power dissipation, speed of operation, Cost. **8**
- b) Design a Full Subtractor using PLA and PAL. **8**
9. a) Elucidate the different types of operators in VHDL. **6**
- b) Write VHDL code for OR gate using case statement. **10**

OR

10. a) What are the different data types in VHDL explain giving example. **10**
- b) If A = "110", B = "111", C = "011000" and D = "111011", compute the following (A & not B or C or 2 and D) **6**
