

USELT02 - Electronics Paper-II (Semiconductor Diodes and Analog Electronics)

P. Pages : 2

Time : Three Hours

**GUG/W/23/11549**

Max. Marks : 50

- Notes :
1. All the questions are compulsory and carry equal marks.
 2. Draw the neat and labelled diagram wherever necessary.
 3. Use of log table/calculator is allowed.

Either:

1. a) What is PN junction diode? Explain the formation of PN junction. 1+4+5
Draw the V-I characteristic of Forward bias PN junction diode and explain it.

OR

- b) What is the breakdown of PN junction? Explain Zener breakdown mechanism? Explain the dc load line analysis of forward bias pn junction diode. 2+4+4

Either:

2. a) What is rectification? Explain half wave rectifier with input and output wave form? Explain the performance parameter I_{dc} and I_{rms} of half wave rectifier. 1+5+4

OR

- b) Draw the circuit diagram of Full wave bridge rectifier and explain the working with input and output wave form? Distinguish between half wave full wave and bridge rectifier. 6+4

Either:

3. a) With the help of circuit diagram explain the input and output Characteristic of CE configuration. What is load line? 8+2

OR

- b) What are the requirements of biasing the transistor? Explain voltage divider method of biasing the transistor? Define stability factor? 4+4+2

Either :

4. a) What is h-parameter? Determine the h_{11} , h_{12} , h_{21} and h_{22} ? 2+8

OR

- b) Draw the hybrid equivalent circuit of CE mode and explain current and voltage gain in CE mode Transistor? 4+6

5. Attempt **any ten** of the followings:

1x10

- a) Define cut in voltage?
- b) What is depletion region?
- c) Draw the circuit symbol of Zener and Schottky diode?
- d) State the disadvantages of full wave bridge rectifier?
- e) What is filter?
- f) Define voltage regulation.
- g) If $\alpha = 0.98$ then find β .
- h) Draw the circuit symbol of PNP and NPN transistor.
- i) What is thermal runaway?
- j) What is the meaning of h parameter h_{re} and h_{fb} ?
- k) What is the Bandwidth of amplifier?
- l) What are the limitation pf h-parameter?
